

Heathkit of the Month:
by Bob Eckweiler, AF6C



AMATEUR RADIO - SWL

Heathkit HW-12 / HW-22 / HW-32

“Single-Bander” SSB Transceivers - PART I

Author’s Note:

I have received many requests to cover the Heathkit *Single-Bander* SSB Transceivers, many more than any other kit. Unfortunately, little was available on the net in the way of manuals and schematics for these six kits. I looked into purchasing the manuals, but the cost was approaching \$200 and these articles are written and distributed without charge as a hobby. Thus, the idea was kept on the back burner, and anytime some information was found, it was squirreled away for later use. One difficulty was that, in the first few partial manuals obtained, no crystal frequency information was given, only their part numbers.

Recently, I felt I had gathered enough information to begin the article. At first, the plan was to cover all six units, while focusing on the HW-22. After working on the article awhile, it quickly became evident it would be very long - much too long for our monthly newsletter. The decision was made to split the article into two, covering the HW-12, HW-22 and HW-32 in the first article and the later HW-12A, HW-22A and HW-32A in a second, shorter article, where only the changes from the earlier models would be covered.

As I continued to write, it was evident the article would still be too long. So the plan now is to cover the HW-12, HW-22 and HW-32 in a multipart series of articles. This might take two or even three parts. Here’s part I:

¹ Notes appear at the end of the article.



Fig. 1 - HW-22 40-meter Transceiver

Introduction:

In late 1963, while I was away at my first year of college, Heathkit introduced three single-band, SSB only, HF ham transceivers. They were the HW-12, the HW-22 and the HW-32 which operate on the SSB portion of the 75, 40 and 20 meter bands, respectively. They each operate in a single mode, LSB for 75 and 40 meters and USB for 20 meters, at 200 watts PEP input. They are powered by an external power supply, such as the HP-23, and can be used in the home or mobile. Over their life they sold for \$119.95 each, and they immediately became big sellers. Orders quickly exceeded Heathkit’s production rates, creating a backlog. Heathkit had a hit on their hands, and I was off the air! Besides appropriate power supplies, Heathkit sold three accessories that work with the HW “Single-Bander” series, a push-to-talk microphone - the GH-12 (\$6.95); a mobile speaker - the HS-24 (\$7.00); and a plug-in 100 kc¹ crystal calibrator - the HRA-10-1 (\$8.95).

The original “Single Bander”^s remained in production for three years, until 1966, when they were replaced by the HW-12A / HW-22A / HW-32A, which were updated and refined versions of the originals. In this series, the focus will be on the earlier transceivers, with the later ones possibly being covered in a future article.

The Heathkit “Single-Bander”:

We will focus on the HW-22 - 40-meter Single-Bander (Figure 1), but will discuss differences between the HW-22 and the HW-12 and HW-32 as they are encountered. The specifications for the radios are exceptional for the selling price (See

Table I). Due to the size of the schematic, it is not included in this article. However snippets of the schematic will be used as needed. A copy of the full HW-22 schematic, found on the web, is posted on the club website at:

<http://www.w6ze.org/Heathkit/Sch/hw22.pdf>.

Heathkit recommended the HP-23² fixed or HP-13³ mobile power supplies for the “Single-Bander” transceivers; these power supplies may be used without modification; just be sure the octal power plug to the HW-12 / 22 / 32 is wired correctly. These radios may also be used with the earlier HP-20 (AC) and HP-10 (DC) power supplies after a simple modification to the radio (and also to the HP-10, if used). Instructions for these modifications are given in the “Single-Bander” manuals.

HW-22 Controls and Connectors:

Except for the frequency dial, the front panel of all three units are identical. On it are nine controls and a meter, arranged in two rows. The top row (L to R) consists of the **FINAL TUNE** capacitor, the large VFO tuning knob with arched tuning window and frequency dial - featuring a seven to one vernier drive - and a meter that operates as an S-meter on receive and a relative output meter on transmit. Below the meter is a slide switch marked **BIAS SET** to the left and **OPERATE TUNE** to the right. The switch is normally in the right position, and is moved to the left to set the bias on the final tubes. In the left position the meter reads the cathode current of the finals. The proper bias setting is marked as a small white triangle above the S-3 mark on the meter scale.

The second row (L to R) consists of a four-position rotary **FUNCTION** switch (**OFF, PTT, VOX, TUNE**), a screwdriver adjustable **S-METER ADJ.** pot, an **RF GAIN** pot, an **AF GAIN** pot, a screwdriver adjustable **VOX DELAY** pot, and a **VOX** sensitivity pot.

Along the rear apron of the HW-22 (L to R, viewed from the rear) are: a two-pin Amphenol **MIC** connector, three screwdriver adjustable

General	
Frequency Coverage (Mode) -	
HW-12	3.8 - 4.0 mc. (LSB)
HW-22	7.2 - 7.3 mc. (LSB)
HW-32	14.2 - 14.35 mc. (USB)
Stability:	200 cps / hr.
# of Tubes (Total Sections):	14 (20)
Cabinet Size:	6-1/4" H x 12-1/4" W x 10" D
Assembled Weight:	12 lbs.
Shipping Weight:	15 lbs.
Power Requirements -	
High Voltage:	800 VDC @ 250 mA peak
B+ Voltage:	250 VDC @ 100 mA
Bias Voltage	-130 VDC @ 5 mA
Filament Voltage:	12 VAC/DC 3.75 A
Transmit	
Power Input:	200 Watts PEP
Finals:	2 x 6GE5
RF Output Z (Loading):	50Ω (Fixed)
Transmit IF:	2,305.0 kc
Carrier Suppression:	45 dB
Unwanted Sideband Suppression:	45 dB
Mic Input:	Hi-Z
Receive	
Sensitivity:	1μV for 15 dB (S + N)/N
Receive IF:	2,305.0 kc
Selectivity:	2.7 kc @ 6dB. 6 kc @ 50 dB
Image Rejection (HW-32):	100 dB (60 dB)
IF Rejection (HW-32):	50 dB (65 dB)
Audio Output:	1 Watt @ 8Ω
Table I: HW-12 / 22 /32 Specifications	

pots (**MIC GAIN, TUNE LEVEL, FINAL BIAS**), four RCA phono connectors (**SPKR 8Ω, EXT. RELAY, ANT., RCVR**), and a male octal **POWER** connector). The EXT. RELAY connection switches to ground on transmit and is open on receive; it is used to key an amplifier or external antenna relay. RCVR is a separate antenna lead that goes directly to the receiver input, and is useful with an amplifier that requires an external antenna relay.

Each model has a different frequency dial behind the arched window. The HW-12 dial tunes up in frequency from 3.8 to 4.0 mc as the tuning knob is turned clockwise. However, the HW-22 and HW-32 actually tune down in frequency as their tuning knob is turned clockwise. The HW-22 tunes 7.3 to 7.2 mc, and the HW-32 tunes 14.35 to 14.2 mc. The frequency dial also shows the model number, which is not printed anywhere else on the front panel.

Heathkit "Single-Bander" Construction:

For each kit, most of the components mount on a single circuit board that holds about 90% of the components, including tubes. Parts not located on the circuit board are controls and other items on the front and rear panels, as well as the audio output transformer, T/R relay and the VFO frequency components that need mechanical stability. Figure 2 shows the top view of an HW-22 removed from its cabinet.

All fourteen tubes, including the final amplifier tubes and the octal socket for the optional 100 kc crystal calibrator accessory, mount on the circuit board. The board itself mounts over a large cutout in the chassis, and takes up most of the top chassis space. A prefabricated and color-coded wiring harness makes almost a full circuit around the edges of the chassis, making connections between the components off the circuit board, as well as connections to the circuit board itself, easier and less prone to wiring errors.

The "Single-Bander" transceivers were designed keeping mobile operation in mind. The cabinet includes a gimbal mount that allows mounting the radio under the dash or on the transmission hump in a typical automobile of the sixties. The manual contains a lot of information on using the "Single-Bander" mobile, including discussions on reducing engine noise and choosing and mounting an appropriate antenna.

Heathkit states that the kit can be assembled in just 15 hours, due mainly to the large circuit board construction. Comments in the reviews



Figure 2: Top view of the HW-22 out of its cabinet. Final tubes are to the left behind vertically mounted pi-network coil. In the back left is the octal socket for the optional crystal calibrator.

agree that the 15-hour claim is easily achieved by a builder with average kit-building competence. Figure 3 is from the March 1965 Heathkit catalog supplement (800/53) offering the "Single-Bander: SSB Transceivers and two of their accessories.

The "Single-Bander" Frequency Scheme:

It is always interesting to study the scheme of how the transmitted and received frequencies are created or recovered; this is especially true in a SSB transceiver since filtering of the desired sideband must occur to generate and receive the signal. The "Single-Bander" transceivers only cover one band, simplifying things. These radios also do not incorporate RIT, which allows the operator to adjust the received signal without changing the transmit frequency. The three models all have an IF of 2,305 kc and use a crystal lattice bandpass filter that is shared on transmit and receive. This filter is not a sealed unit like in the SB series, but consists of two pairs of matched crystals, and their associated components, assembled on the circuit board. The filter has a center frequency of 2,305.0 kc with a 6 dB bandwidth between 2,303.7 and 2,306.4 kc, and a 50 dB bandwidth between 2,302.0 and 2,308.0 kcs. (See Figures 4A & 4B)

The Finest In Ham Radio Kits!



- Operate SSB on either 80, 40, or 20 meters
- 200 watts P.E.P. input • LSB on 80 & 40, USB on 20 • Crystal filter SSB generation • Complete transceiver operation • ALC, AVC, and S-meter • Built-in VOX & push-to-talk circuitry
- Stable low frequency VFO • 2 kc dial calibration—6" bandspread—vernier tuning

Heathkit "Single-Bander" SSB Transceivers

Compact, Lightweight, Uncluttered Styling . . . make these units ideal for mobile operation or for that "corner of the living room" station. Necessary accessories are antenna, power supply, speaker, microphone, and crystal calibrator . . . see below!

Features To Delight Any Amateur! Include a deluxe 14-tube superheterodyne receiver with 1 uv sensitivity, 2.7 kc selectivity, and slow AVC action . . . provision for simple plug-in connection of HRA-10-1 100 kc crystal calibrator (optional) for accurate band-edge markings. Features assure excellent SSB reception! 200 watts of PEP input power cuts through QRM. Built-in VFO is in the 1.5-1.8 mc. range, and temperature compensated for high stability. VOX circuit permits "no hands" operation. Automatic level control gives the audio real sock! The "Single-Bander" you choose will give you many "5 by 9" reports. **Designed For Fast, Easy Assembly!** Heavy-duty circuit board and pre-cut wiring harness cut average wiring time to only 15 hours. Order your "Single-Bander" today.



Kit HW-12: 80-meter, 15 lbs. . . \$12 dn., \$11 mo. \$119.95
 Kit HW-22: 40-meter, 16 lbs. . . \$12 dn., \$11 mo. \$119.95
 Kit HW-32: 20-meter, 15 lbs. . . \$12 dn., \$11 mo. \$119.95
 GH-12, Push-to-talk and VOX microphone . . . 2 lbs. \$6.95
 Kit HRA-10-1, Plug-in kc crystal calibrator . . . 1 lb. \$8.95

HW-12 SPECIFICATIONS—RF input: 200 watts PEP. Sideband generation: Crystal lattice bandpass filter method. Stability: 200 cps per hour after warm-up. Carrier & unwanted sideband suppression: 45 db. Frequency coverage: HW-12, 3.8—4.0 mc; HW-22, 7.2—7.3 mc; HW-32, 14.2—14.35 mc. Receiver sensitivity: 1 uv for 15 db (S+N); N ratio. Receiver selectivity: 2.7 kc @ 6 db, 6.0 kc @ 50 db. Output: 50 ohm fixed (unbalanced). Operation: HW-12 & HW-22, LSB; HW-32, USB. Audio output: 1 watt @ 8 ohms. Mike input: Hi-Z. Panel controls: Frequency, final tune, function (OFF-PT-VOX-TUNE), RF gain, AF gain (pull for crystal calibrator), VOX gain, meter. Front panel screw-driver adjust for S-meter and VOX delay. Rear panel controls: Mike gain, tune level, final bias. Tube complements: Fourteen tube heterodyne circuit; (3) 6EAB's mic. amp., VOX relay amp., IF amp., RF amp., Recvr. mixer; (5) 6AU6's, VFO, VOX amp., IF amps., Xmtr. mixer; (1) 6BE6, VFO isolator (HW-12), Het. osc. and mixer (HW-22 & HW-32); (1) 12BY7 Driver; (1) 12AT7 Xtal. osc., product det.; (1) 6EB8 Audio amp. and output; (2) 6GE5 RF output. Power requirements: 800 VDC @ 250 MA peak, 250 VDC @ 100 MA, —130 VDC @ 5 MA, 12 VAC or VDC @ 3.75 amperes. Cabinet dimensions: 5 1/4" H x 12 1/2" W x 10" D.

Figure 3: Heathkit ad for the HW-12, HW-22 and HW-32 in the March 1965 Catalog supplement.

Each model's VFO operates on a different range of frequencies, but all are within 1,400 to 1,800 kc. Using such a low frequency aids in designing a stable VFO; a temperature compensating capacitor further increases the stability. Each VFO's fully clockwise and counterclockwise frequencies are shown in Table II. The transmit frequencies shown are the frequency where the carrier would be if it were not suppressed.

The stage following the VFO varies between models. For the 75-meter HW-12, the stage acts as a buffer, isolating the load from the VFO; however, on the HW-22 and HW-32 this stage is a heterodyne crystal oscillator and mixer. The oscillator runs at 11,190.0 and 18,275.0 kc respectively. The mixer output is the difference between the heterodyne oscillator and VFO, as shown in Table II. Since this is a difference mixer the VFO tuning direction is reversed.

On Transmit (See block diagram - Fig 5):

Each "Single-Bander" carrier oscillator uses either a 2,303.3 kc crystal for USB generation or a 2,306.7 kc crystal for LSB generation. This signal is mixed with the transmit audio in a balanced modulator, producing a double sideband signal. This DSB signal is passed through the crystal lattice bandpass filter, and one of the two sidebands is removed. Since the carrier frequency is also outside the 6 dB filter bandpass, any residual carrier from the balanced modulator is also further attenuated. The HW-12 and HW-32 both use a 2,306.7 kc crystal and create an LSB signal, and the HW-22 uses a 2,303.3 kc crystal and creates a USB signal. It would appear the HW-22 and HW-32 sideband are both incorrect, but they will be inverted in a later stage. Figures 4A and 4B show the filter response in black, the already suppressed carrier in red, the low audio (400 cps) in orange and

RADIO		VFO CCW	VFO CW
HW-12	VFO Freq:	1,493.3	1,693.3
	Buffer Out:	1,493.3	1,693.3
	Carrier (LSB):	2,306.7	2,306.7
	Mixer (sum):	3,800.0	4,000.0
	Final Sideband:	LSB	
HW-22	VFO Freq:	1,586.7	1,686.7
	Het. Xtal Osc:	11,190.0	11,190.0
	Het. Mixer Out:	9,603.3	9,503.3
	Carrier (USB):	2,303.3	2,303.3
	Mixer (Diff.):	7,300.0	7,200.0
	Final Sideband:	LSB	
HW-32	VFO Freq:	1,618.3	1,768.3
	Het. Xtal Osc:	18,275.0	18,275.0
	Het. Mixer Out:	16,656.7	16,506.7
	Carrier (LSB):	2,306.7	2,306.7
	Mixer (Diff.):	14,350.0	14,200.0
Final Sideband:	USB		
All frequencies are in kilocycles per second			
Table II: Transmitter Frequencies			

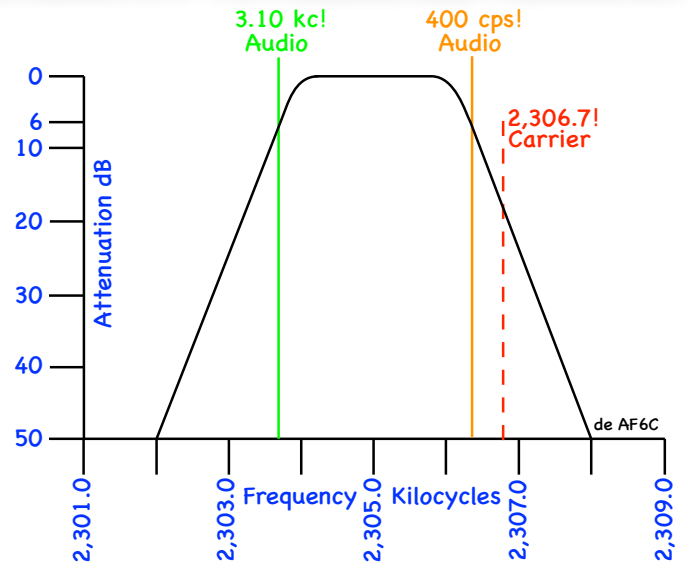


Fig. 4B: Lower sideband creation in the crystal filter. The upper sideband is to the right, outside the filter's response.

HW-12 it is added to the the buffered VFO frequency in the transmitter mixer stage, producing an LSB output between 3.8 and 4.0 mc. In the HW-22 and HW-32 the SSB signal is subtracted from the heterodyne mixer output in the transmitter mixer stage; the sideband is inverted during this mixing process. This results is an LSB output between 7.3 and 7.2 for the HW-22,

the high audio (3,100 cps) in green for the desired sideband.

After filtering, the 2,305.0 SSB signal is converted to the desired transmit frequency. In the

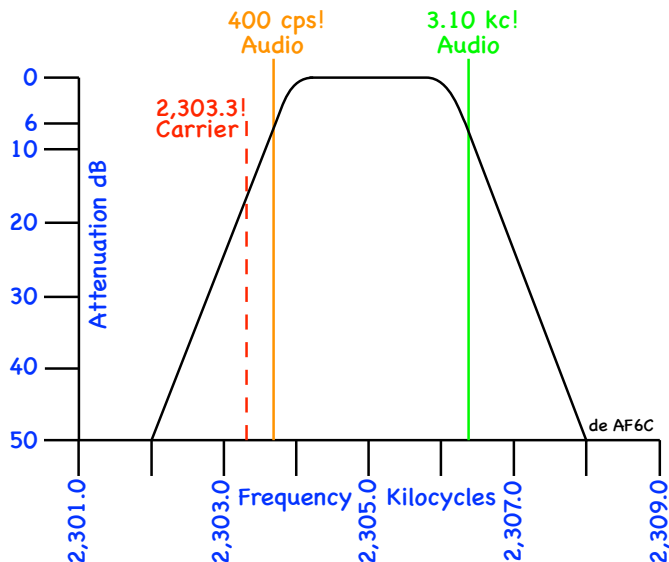


Fig. 4A: Upper sideband creation in the crystal filter. The lower sideband is to the left outside the filter's response.

Radio		VFO CCW	VFO CW
HW-12	Rcvd Freq (LSB):	3,800.0	4,000.0
	VFO Buffer Out:	1,493.3	1,693.3
	Rcvr Mixer Out (LSB):	2,306.7	2,306.7
	Carrier (LSB)	2,306.7	2,306.7
HW-22	Rcvd Freq (LSB):	7,300.0	7,200.0
	Het. Mixer Out:	9,603.3	9,503.3
	Rcvr Mixer Out: (USB):	2,303.3	2,303.3
	Carrier (USB)	2,303.3	2,303.3
HW-32	Rcvd Freq (USB):	14,350.0	14,200.0
	Het. Mixer Out:	16,656.7	16,506.7
	Rcvr Mixer Out: (LSB):	2,306.7	2,306.7
	Carrier (LSB):	2,306.7	2,306.7
Table III: Receiver Frequencies			

and a USB output between 14.35 and 14.20 for the HW-32.

A good way to examine what is going on more closely is to track two tones as they are transmitted and later received. We'll use the HW-22 for this example with its VFO set for 7,250 kc. A good choice of tones are 400 cps and 3.1 kc as they represent the 6 dB points in the filter. These tones are fed into the microphone input, are amplified and mixed with the carrier in the balance modulator. The four outputs of the balanced modulator are the 2,303.3 kc carrier oscillator plus and minus each of the tones or: 2,300.2, 2,302.9, 2,303.7 and 2,306.8 kc. The 2,303.3 carrier has been balanced out does not appear in the output. These four tones are fed into the crystal filter and only two remain - 2,303.7 and 2,306.4 kc. (see figure 4A).

Meanwhile, if we are transmitting with the VFO set to 7,250.0 kc, the VFO is tuned to actually produce a frequency of 1,636.7 kc. which is mixed with the 11,190.0 kc crystal heterodyne oscillator producing outputs of 9,553.3 and 12,826.7 kc as well as the two original frequencies. L5 is tuned so it passes only the 9,553.3 kc difference signal. This is true during receive also.

In the transmitter mixer, the 9,553.3 kc frequency is mixed with the two signals from the crystal filter, after they are amplified. L2 passes only signals within the 40 meter band. These are the two difference frequencies 9,553.3 - 2,303.7 and 9,553.3 - 2,306.4, or 7,249.6 and 7,246.9 kc. Note that these two frequencies are 0.4 and 3.1 kc below the tuned frequency showing that they are LSB components of a 7,250.0 transmitted signal. These two frequencies are further amplified and sent to the antenna.

On Receive (See block diagram - Fig 6):

During receive, the incoming RF signal is first amplified and then mixed in the receiver mixer stage with the same heterodyne signal used by the transmitter mixer. As a result, the received signal is converted to the 2,305.0 kc IF frequency, and the sideband is inverted on the

HW-22 and HW-32. The IF signal then passes through the crystal filter where only the desired sideband is passed. From here it is amplified and finally mixes with the same carrier oscillator used for transmit. The result is audio in the 400 cps to 3.1 kc range. The resulting frequencies are shown in Table III.

Continuing the exercise of tracking the 0.4 and 3.1 kc tones at the receiving end - if the receiver is tuned to 7,250 kc the two signals at 7,249.6 and 7,246.9 are amplified by the receiver RF amplifier and fed to the receiver mixer where they are mixed with the same 9,553.3 signal as during transmit. The difference frequencies are 2,303.7 and 2,306.4 kc, and the sideband is inverted back to USB. These two signals pass through the filter, while signals outside the bandpass are removed, or heavily attenuated. This includes any interference that might be in the other sideband's frequency range. The two signals are then amplified in the IF amplifiers and mixed in the product detector, with the crystal carrier oscillator oscillating at 2,303.3 kc. Only the audio frequencies are passed on to the audio stages, while RF frequencies are bypassed to ground. The results are 2,303.7 - 2,303.3 and 2306.4 - 2,303.3 kc or 0.4 and 3.1 kc. which are the original tones sent, and are now being heard in the receiver speaker.

Service Bulletins:

Heathkit put out several service bulletins on the HW-12/22/32. to increase stability and other improvements. Filament and other bypassing is improved, especially around the VFO. A small 0.001 capacitor is added between the mic amplifier and ground on the two higher frequency radios to curb RF getting into the audio. Bias voltages are tweaked by a resistor change and finally, on all three units, one of the bias resistors is replaced by a higher wattage resistor.

In another service bulletin, specific to the HW-32, coil cans L5 and T2 are connected together with heavy bare wire to prevent a ground-loop. T3, L2 and L3 are likewise connected. Here is a link to these mods:

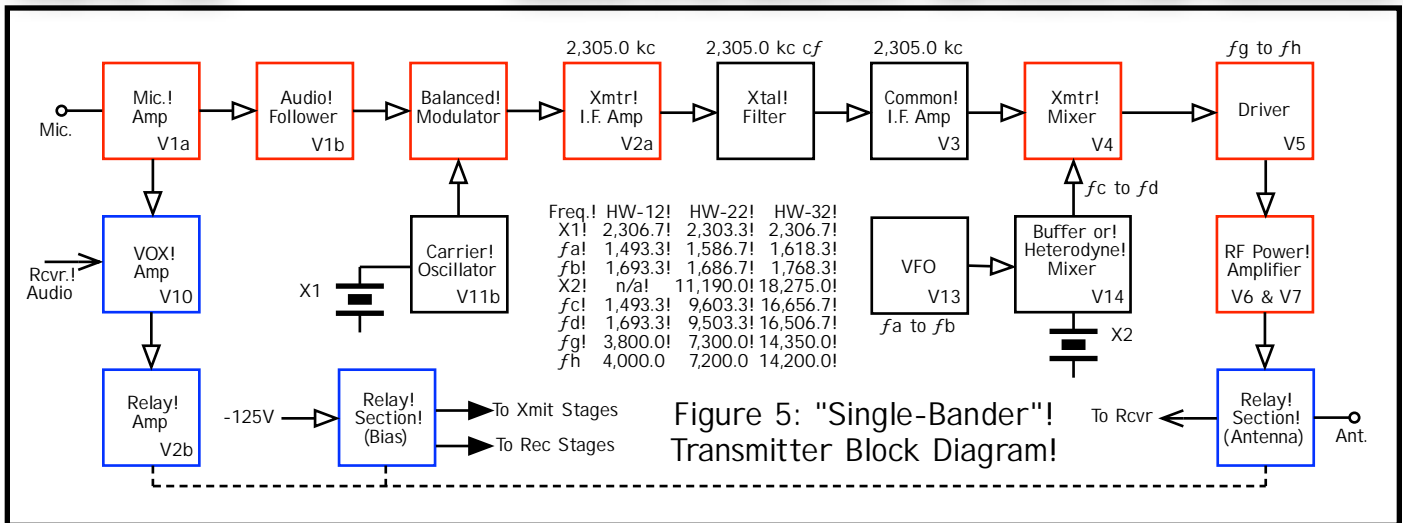


Figure 5: "Single-Bander"! Transmitter Block Diagram!

<http://www.w6ze.org/Heathkit/TN/hw22.pdf>

Comments:

In the July 1964 Heathkit catalog there was a "Special value price" of \$310 for the HW-42. This was a package deal for all three transceivers I don't know how long it lasted, but I never saw it offered in any later catalog that I have access to.

In the next article we'll discuss the general tube line-up and delve into the transmitter circuitry, and if space permits, cover the receiver circuitry as well.

Notes:

- 1 When this kit was released kc - kilocycle [per second] was the common term used. KHz - Kilohertz was still to be adopted. I try to use the terms that existed when the kits were introduced.
- 2 HP-23 Series, see HOM #26 - Mar. 2011
- 3 HP-13 Series, see HOM #40 - Jun. 2012

HOM (Heathkit of the Month) Articles are available at: http://www.w6ze.org/Heathkit/Heathkit_Index.html

This article originally appeared in the February 2016 issue of RF, the newsletter of the Orange County Amateur Radio Club - W6ZE.

Remember, if you are getting rid of any old Heathkit Manuals or Catalogs, please pass them along to me for my research.

Thanks - AF6C

73, from AF6C

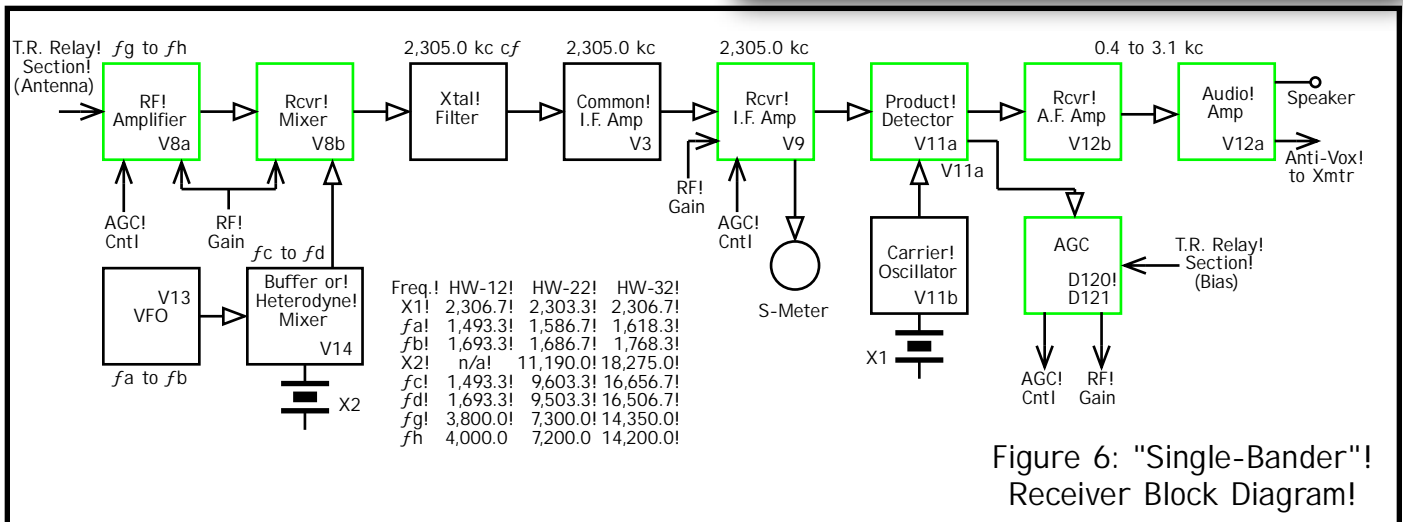


Figure 6: "Single-Bander"! Receiver Block Diagram!

Heathkit of the Month:
by Bob Eckweiler, AF6C



AMATEUR RADIO - SWL
Heathkit HW-12 / HW-22 / HW-32
“Single-Bander” SSB Transceivers - PART II

Introduction:

in the February issue of *RF* the “Single Bander” HW-12 (75 meters LSB), HW-22 (40 meters LSB) and HW-32 (20 meters USB) were the topic. These sideband only transceivers were very popular in the mid sixties; many are still on the air today. In the February article the construction, control layout and frequency scheme were discussed at length. This month the circuit will be covered.

Since the schematics are too big to publish here, a copy of the HW-22 schematic has been uploaded to our website so you can follow everything a little closer:

<http://www.w6ze.org/Heathkit/Sch/hw22.pdf>.

Schematics of the other “Single Bander”s may be available on line too, but the HW-22 is representative of the other radios and should suffice. Snippets of the schematics of the other radios may be used as needed.

Figures 5 and 6 are block diagrams of the transmitter and receiver sections (Table and figure numbers will continue from last month. If one is shown in both articles, it will retain its original number.)

Tube Line-up:

Each of the “Single Bander” transceivers uses 14 tubes; with the exception of V14, they each perform the same function in each radio. Five of the tubes are dual-section, so the effective tube count is 19, and even 20 on the HW-22 and HW-32 if you consider the dual function for V14 tube.



Fig. 1 - HW-22 40-meter Transceiver

ID	Section - Tube # (Type)	Function
V1A	1/2 - 6EA8 (P)	Mic Amp
V1B	1/2 - 6EA8 (T)	Audio Follower
V2A	1/2 - 6EA8 (P)	Xmtr IF
V2B	1/2 - 6EA8 (T)	Relay Amp
V3	6AU6	Common IF Amp
V4	6AU6	Xmtr Hetro. Mixer
V5	1/2 - 6EA8 (P)	Xmtr RF Driver
V6	6GE5	RF Power Amp
V7	6GE5	RF Power Amp
V8A	1/2 - 6EA8 (P)	Rcvr RF Amp
V8B	1/2 - 6EA8 (T)	Xmtr Het. Mixer
V9	6AU6 (P)	Rcvr IF Amp
V10	6AU6 (P)	VOX Amp
V11A	1/2 - 12AT7 (T1)	Product Detector
V11B	1/2 - 12AT7 (T2)	Carrier Oscillator
V12A	1/2 - 6EB8 (P)	Rcvr Audio Out
V12B	1/2 - 6EB8 (T)	Rcvr Audio Amp
V13	6AU6 (P)	VFO
V14 ¹	6BE6 (H)	VFO Follower
V14 ²	6BE6 (H)	VFO Het Osc/Mix

¹ HW-12 75-meter transceiver only
² HW-22 40-meter & HW-32 20-meter transceivers
Tube Type: (P) = Pentode, (H) = Heptode, T = Triode

TABLE IV – “Single Bander” Tube Line-up

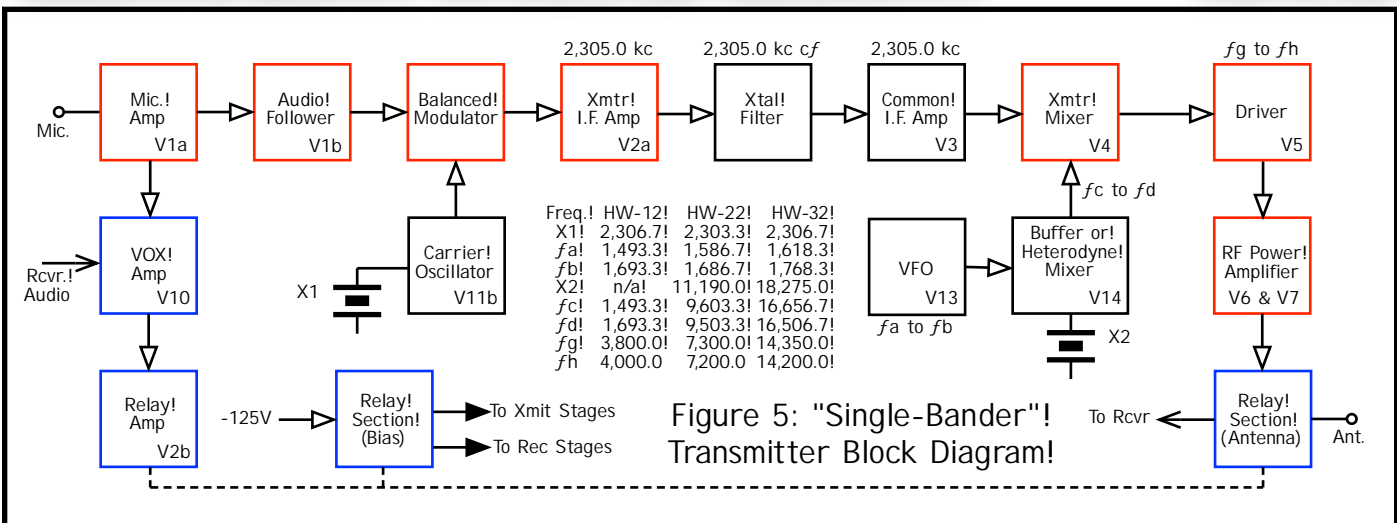


Figure 5: "Single-Bander"! Transmitter Block Diagram!

Circuit Description:

The circuit may be broken up into four sections - the oscillators, the transmitter, the receiver and the transmit/receive control and switching.

The Oscillators:

All three radios have a similar crystal controlled carrier oscillator and VFO oscillator. The HW-22 and HW-23 also have a crystal controlled heterodyne oscillator to raise the frequency of the VFO without compromising stability. All three oscillators use series-resonant crystal mode oscillators.

Carrier Oscillator (V11B):

The crystal controlled carrier oscillator uses 1/2 of a 12AT7 in a Colpitts oscillator circuit. It operates either on a frequency of 2,303.3 or 2,306.7 kc. Each frequency is 1.70 kc from the

2,305.0 kc IF frequency. The lower crystal frequency will initially create an USB signal after passing through the crystal filter; likewise, the higher crystal frequency will create an LSB signal. Feedback is supplied by the series capacitors and the signal is taken from the cathode. This oscillator provides the carrier signal to the balanced modulator on transmit, and carrier injection signal to the product detector on receive.

VFO Oscillator (V13):

A 6AU6 pentode is used to generate the VFO signal. This is also a Colpitts circuit. Since the frequency range and frequency span of the VFO is different for each of the "Single-Bander" radios, the capacitor values, including the variable capacitor are not identical across the line. The lower and upper range of the VFO is given in Figures 5 or 6 as fa and fb.

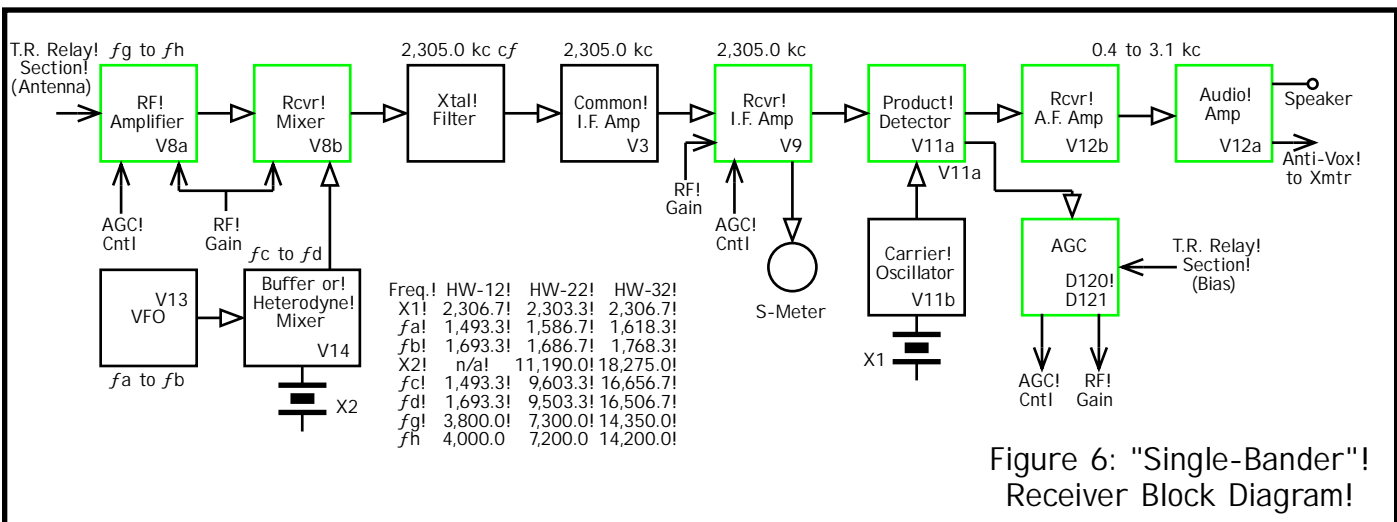


Figure 6: "Single-Bander"! Receiver Block Diagram!

The same coil is used in each (L5 in the HW-12 and L6 in the HW-22 and HW-32), and is temperature compensated by C130, a negative temperature coefficient capacitor. The remaining frequency determining capacitors are of the NPO type. Using a low frequency around 1,600 kc for the VFO adds to the stability, as does mounting the coil and variable capacitor on the rigid chassis instead of the circuit board.

VFO Buffer (V14) [HW-12 only]:

Since the HW-12 uses the VFO frequency as the transmitter and receiver mixer frequency directly, it does not need to be heterodyned to a higher frequency. However, to keep load changes from pulling the VFO off frequency, V14 acts as an isolation buffer in the form of a cathode follower. Evidently Heathkit wanted to use the same tube lineup for all the “Single-Bander”s, so a 6BE6 pentagrid tube that is used as a heterodyne oscillator and mixer in the higher frequency radios, is used as a triode cathode follower in the HW-12. The schematic of this circuit, along with the VFO oscillator, is shown in figure 7. Note that there is no connection to the plate (pin-5) of the tube; instead, the first screen grid acts as the plate. The signal from the VFO is coupled to the 1st control grid (pin-1). Since the two screen grids (pin-6) are connected internally, the second control grid (pin-7) is tied to the first one externally. In effect this creates a triode. The buffered signal appears at the cathode (pin-2) where it is fed to the receiver mixer and, after filtering (not shown in figure 7), to the transmitter mixer. Capacitor C134 is large enough to bypass any harmonics to ground while passing the fundamental frequency to the buffer.

Heterodyne Oscillator & Mixer (V14)

[HW-22 & HW-32]:

In the two higher frequency radios, the VFO is raised in frequency by mixing it with the signal from a crystal oscillator. This raises VFO frequency without introducing additional drift of any significance. V14, a pentagrid tube (five grids), also called a heptode (seven electrodes), is a tube designed specifically as a single tube

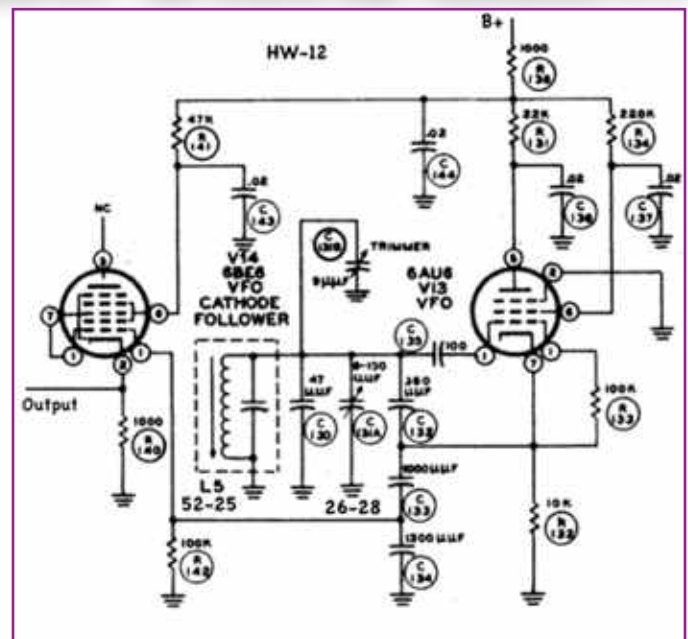


Figure 7: HW-12 (75-Meter) VFO with Buffer

that functions as an oscillator and mixer. The first grid is a control grid for the oscillator; in this case another crystal Colpitts oscillator. The second grid acts as a plate for the oscillator section; it is connected to the screen source. Since this grid is so porous, some electrons pass right through to the second section. The third grid is also a control grid. The VFO signal is coupled to it. The fourth grid, which is internally connected to the second grid, is a screen grid for the upper section, and the fifth grid is a suppressor grid to absorb any electrons bouncing off the plate. With the tube biased to a point where it is no longer linear, mixing occurs and the two frequencies, plus their sum and difference appear at the plate. L5 is broadly tuned to the difference frequency band. The heterodyne crystals are at 11,190.0 (HW-22) and 18,275.0 kc (HW-32), resulting in output frequencies between f_c and f_d (Fig. 5 or 6) as the VFO is tuned.

The TRANSMITTER:

Microphone Amplifier (V1A):

Audio from a high impedance microphone is amplified by V1A, the pentode section of a 6EA8. C11 removes any RF entering from the mic connection. This is a simple pentode amplifier using grid-leak biasing. Its output is fed

to the MIC GAIN control. The low end of the control is AC coupled to ground so the next stage can be biased off during transmit.

AF Cathode Follower (V1B):

The triode section of the 6EA8 is a cathode follower buffer. It presents a low output impedance audio signal to the balanced modulator through C18.

Balanced Modulator (CR1 - CR4):

Mic audio from V1B is mixed with the carrier oscillator signal in the balance modulator (Figure 8). The RF carrier signal is fed across R8 to the junction of two legs of the bridge consisting of C1 & R3 and C2 & R4. When these legs are identical, the bridge is balanced and none of the carrier signal appears across transformer.- T1's primary. The CARRIER-NULL control adjusts the bridge balance, correcting for component tolerances. When audio is applied from V1B to the diode ring, it unbalances the bridge at an audio rate, causing the upper and lower sideband signals to appear across the transformer primary. In order to provide a carrier for tune-up, the TUNE LEVEL places a DC voltage across the diode ring when the FUNCTION switch is in the TUNE position, resulting in an unbalancing of

the bridge, allowing a steady carrier to appear across T1.

Transmitter IF Amplifier (V2A):

V2A, the pentode section of a 6EA8, amplifies the two sideband signals from the secondary of T1 and applies them to the crystal filter. It also matches the impedance the filter needs to see for optimal performance.

Crystal Filter (Y2 - Y5):

The crystal filter passes only the desired sideband for the particular model, which is determined by the carrier oscillator crystal and whether sideband inversion occurs later in the transmitter mixer. Y2 through Y5 are matched pairs of crystals at 2,303.5 and 2,505.1 kc., which, along with L1, provide a filter response as shown in figures 8. With a carrier crystal of 2,303.3 kc (red) the filter passes only the USB signal within an audio range of 400 to 3,100 cps at the 6 dB points (shown green to yellow), which corresponds to 2,303.7 to 2,306.4 kc. Similarly, with a carrier crystal of 2,306.7 kc (purple) the filter passes only the LSB signal within an audio range of 400 to 3,100 cps, which corresponds to 2,306.4 to 2,303.7 kc. This signal is then coupled to V3, the common IF stage.

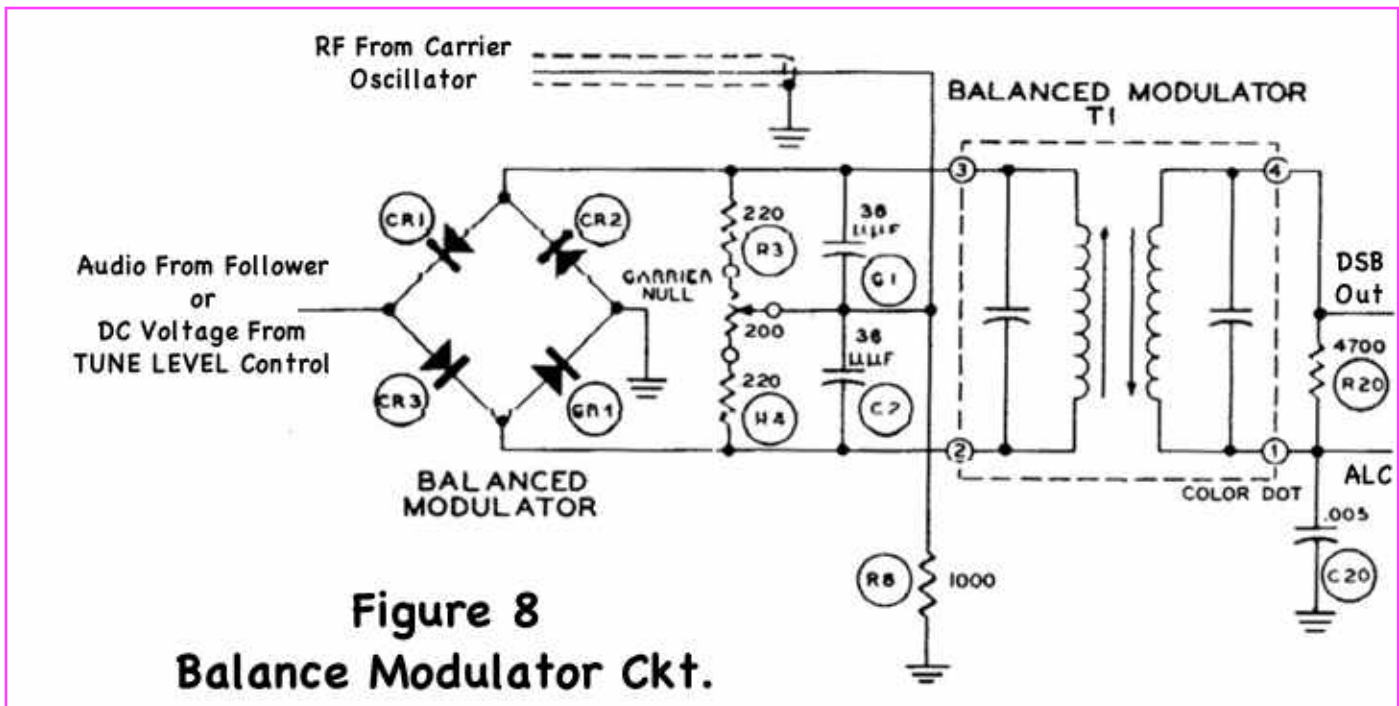


Figure 8
Balance Modulator Ckt.

The Common IF (V3 - During Transmit):

The common IF uses V3, a 6AU6 pentode, It is driven directly from the crystal filter, with R30 providing the proper load for the filter. Output is through a double tuned IF transformer, T2. This stage and the filter are used for receiving also.

Transmitter Mixer (V4):

In the transmitter mixer, another 6AU6 pentode, the transmitter IF signal and the heterodyned (or buffered in the case of the HW-12) VFO signal from V14 are mixed. Only one of the mixer products is allowed to pass the double tuned driver grid transformer L2. The heterodyne signal is coupled to the secondary of T2, along with the transmitter IF, and both are fed to the control grid of V4. On the HW-12 the sum of the two signals is passed and no sideband inversion occurs. But, on the HW-22 and HW-32 the difference between the two signals is passed. Since the sideband signal is subtracted from the higher frequency oscillator signal, sideband inversion does occur. To correct for this, the carrier oscillator crystal is selected to initially produce the other sideband.

Driver (V5):

The driver tube is a 12BY7 power pentode. It operates as a linear, tuned grid, tuned plate power amplifier. It is broadly tuned to operate over the desired band segment and no front panel tuning adjustment is provided. A small part of the RF energy from the final amplifier stage (discussed next) is fed back through a capacitive voltage divider consisting of capacitors C63, C64 and C55 to the B+ side of the plate coil L2. This voltage provides fixed neutralization for the final amplifiers.

Final Amplifier (V6 & V7):

A pair of 6GE5 "Compactron" beam-power tubes, originally designed for TV horizontal sweep deflection amplifiers, provide 200 watts of input power. The tubes are effectively in parallel with their plate, control grid and cathode connected together, and their screen grids fed by separate resistors. RF is capacitively coupled from L2 to the grids. The pi-network output

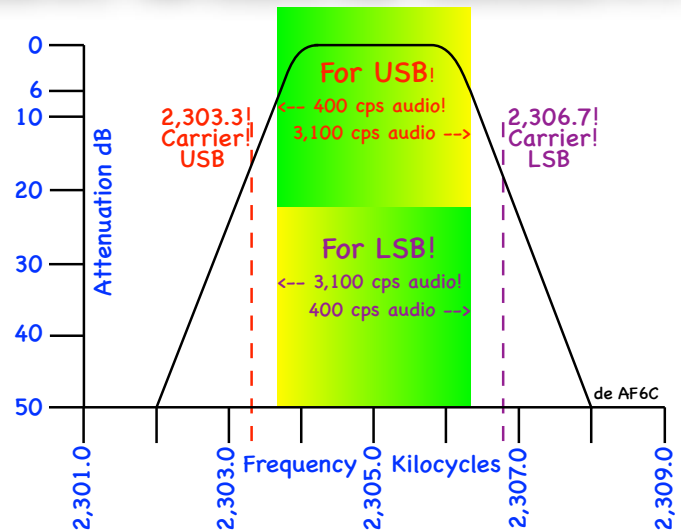


Figure 9: Filter Frequency Response (See Text)

circuit is simple since there is no band switching; L4 provides the tuning inductance. The only adjustment is the FINAL TUNE capacitor; loading is fixed by C77 for use with a 50Ω load. Low value capacitors C61 and C71, along with the circuit board trace, provide VHF oscillation suppression.

Final bias is provided through a voltage divider chain from the -130-volt power connection. The FINAL BIAS control allows setting the resting plate current to the proper value.

ALC (D70):

To help prevent the transmitter from becoming non-linear ALC (Automatic Level Control) is provided. Should the amplifier be over driven, the grid will start to draw current. This causes fluctuation in the grid voltage at the audio rate. This AC voltage is coupled through C75 and rectified by D70. The resulting negative DC voltage increases the bias on V2A (the Xmtr IF) V4 (the Xmtr mixer) and V5 (the driver), reducing their gain and bringing the final amplifier back into linearity.

The RECEIVER:

RF Amplifier (V8A):

When in receive mode, the antenna, and the signal from the optional 100 kc crystal calibra-

tor, if installed and turned on, are fed to the a coupling link on L3, the driver plate tuning coil. The driver plate tuning coil is also coupled to the grid of the RF amplifier V8A, the pentode section of a 6EA8. In a similar fashion the plate of the RF amplifier shares the double tuned driver grid coil L2. This eliminates the need for two additional coils and simplifies alignment.

Receiver Mixer (V8B):

V8B, the triode section of a 6EA8, acts as a simple mixer. The signal from the RF amplifier is fed to the grid; and the heterodyne signal from V14 is fed across the cathode resistor; this signal is 2,305.0 kc above or below the desired receive frequency, depending on the model. The plate signal is coupled to the common IF stage where only the output of the mixer at the 2,305.0 kc IF frequency is allowed to pass.

The Common IF (V3 - During Receive):

The common IF is used for both transmit and receive. It consists of the crystal filter, followed by an IF amplifier using a 6AU6 pentode and a double-tuned coupling transformer T2. The crystal filter is centered around the 2,305.0 kc IF frequency, and was discussed under the transmitter section. The filter is just wide enough to pass an SSB signal. On receive, T2 acts only as a single tuned circuit and the IF signal is capacitively coupled from the plate of V3 to the receiver IF stage, V9.

The Receiver IF (V9)

The receiver IF is the second stage of IF amplification using a 6AU6 pentode. This is a typical IF stage and the amplified IF signal is fed through a double-tuned IF transformer to the grid of V11A, the product detector

The Product Detector (V11A)

The product detector is another mixer; it uses a triode section of a 12AT7, V11A. It recovers the audio from the IF signal fed to the grid by beating it against the carrier oscillator signal which is coupled across the cathode resistor R112. If the IF signal is the correct sideband and tuned properly,

the difference between these two signals is a reproduction of the transmitted audio. The unwanted higher frequency mixer components are bypassed to ground through C111 and C112.

The Receiver 1st Audio (V12B)


The first audio stage is a common class A triode audio amplifier. It amplifies the audio and passes it to the audio power amplifier. This stage also provides an AVC (automatic volume control) voltage to the AVC circuit (discussed later).

The Receiver AF Output Amp (V12A)

The audio from the previous stage is amplified in a class A power stage, and transferred via the audio output transformer, T4, to an external 8Ω speaker. The cathode circuit is a bit unusual; R120 develops bias for the tube while C120 rolls off the low frequencies below 160 cps. The choke coil (RFC-120) presents a higher impedance to the higher frequency audio components, which are then fed back to V12B providing degenerative feedback, canceling the higher frequency audio components, some of which may be noise.

AVC Circuit (D120 & D121)

The AVC (Automatic Volume Control) circuit, also sometimes referred to as AGC (Automatic Gain Control) reduces the gain of the RF amplifier, receiver IF and the audio output stage when a strong signal is received. A sampling of the received signal, isolated by R128, is coupled to two crystal diodes (D120 and D121) that, in conjunction with C121 and C88, form a negative voltage doubling rectifier. C121 charges quickly, providing fast gain reduction, while C88 discharges slowly providing delayed recovery for proper SSB reception. The AVC voltage is fed to the RF amplifier directly, while lower voltages are tapped off to control the receiver IF and 1st audio stages. This divider string is returned to the cathode of the 1st audio stage, providing a slight positive voltage during weak reception, canceling and AVC action due to noise and improving the weak signal sensitivity. As part of the transmit - receive

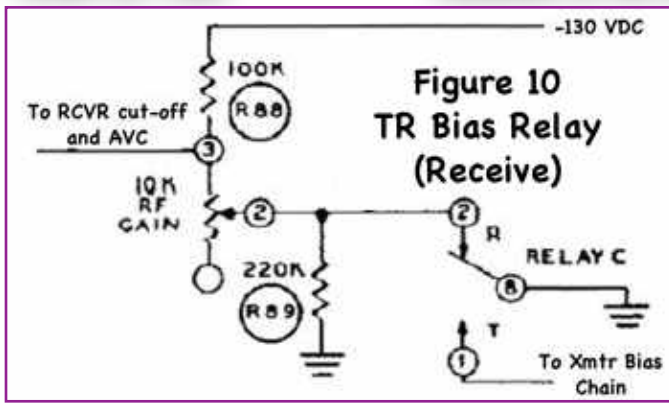


switching circuitry, to be discussed next, a high negative voltage is applied to the AVC line during transmit, effectively cutting these three stages off.

TRANSMIT/RECEIVE Switching:

T/R Relay:

A 3-pole relay controls whether the transceiver is in transmit or receive mode. One of the poles switches the antenna between the RF amplifier during receive, and the pi-network during transmit. The second section controls an external contact that is open during receive and grounded during transmit, allowing the user to switch an amplifier or use otherwise as desired. The third contact switches the bias on various stages, biasing them heavily off when they are not in use. The relay is controlled either by the VOX (Voice Operated Xmit) circuit or the PTT (Push-to-Talk) circuit, depending on the setting of the front panel FUNCTION switch.

A resistor divider chain from the -130-volt power connection to ground, consisting of R88, the RF gain control and R89, provides bias to the receiver mixer and the low end of the receiver AVC line (Figure 9). During receive, the wiper of the RF GAIN control is grounded, and the bias voltage on the receiver cut-off bias line is determined by the position of that control. The line goes to the low end of the AVC circuit adding to any AVC created bias, and the gain of V8A, V9 and V12A decrease as the pot is turned CCW. On transmit the ground is removed from the RF GAIN control and the RCVR cut-off line bias jumps to negative 90 V. This voltage is

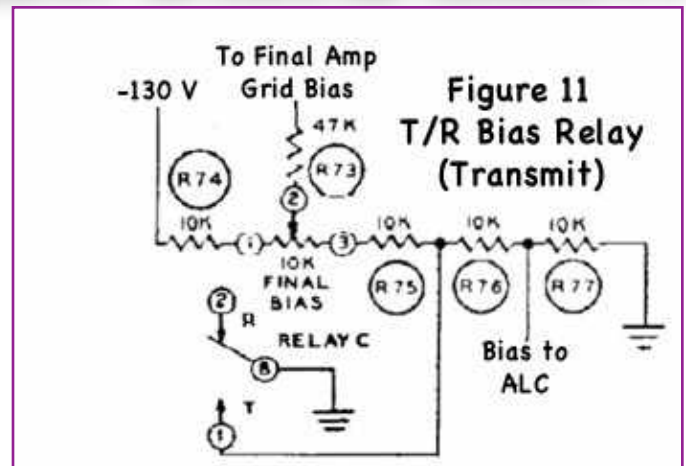

added to the low end of the AVC line forcing all the tubes affected by the AVC into cutoff. This line also directly biases off V8B, the receiver mixer stage, effectively turning the receiver off.

Another resistor voltage divider chain from the -130-volt power connection to ground consists of R74, the final bias potentiometer, R75, R76 and R77 (Figure 10). This places a large bias on the ALC controlled stages as well as the final amplifier and mic audio follower, forcing them into cutoff. When the relay activates, the junction of R75 and R76 is brought to ground potential, restoring normal operating bias on the finals, and other transmitter stages, switching the radio to transmit.

Relay Amplifier (V2B):

The T/R relay is controlled by the relay amplifier. V2B, the triode section of a 6EA8, is normally biased off by the negative voltage from the VOX DELAY control. When the FUNCTION switch is in TUNE the grid is grounded and current flows in the tube causing the relay to activate. If the FUNCTION switch is in the PTT or VOX positions, pressing the PTT microphone switch also grounds the grid of V2B, causing the relay to activate.

VOX Amplifier (V10):

Pentode V10, a 6AU6 pentode, is normally biased on. A large plate resistance results in the plate voltage being very low. In the PTT position the control grid is grounded keeping the tube from responding to any input. When the FUNC-

TION switch is moved to the VOX position the ground is removed from the grid and capacitor C105 is switched into the circuit. When microphone audio is present at the plate of the mic amplifier (V1A) it is coupled to the grid of the VOX amplifier. The negative audio peaks reduce the current flow in the tube causing the plate voltage to rise at each peak. The high plate voltage fires the neon bulb, sending a pulse to the grid of the relay amplifier, causing the relay to close. This pulse also charges C105 which holds the relay amplifier tube on and the relay closed. After a delay, determined by the bias set by the VOX DELAY control, C105 discharges and the relay opens, switching to receive.

ANTI-VOX (D100):

Receive audio, from the plate of the audio output amplifier (V12A), is rectified by diode D100. The resulting positive voltage is filtered and fed to the wiper of the VOX control. This positive voltage bucks any negative voltage that the microphone picks up, preventing speaker audio from tripping the relay. The VOX control is a single control that not only adjusts the anti-VOX, but also, since it acts as a voltage divider to the mic audio reaching V12A, acts as a sensitivity control for the VOX.

Comments:

The HW-12/22/23 became popular for mobile operations as well as use in the shack. If 100 watts mobile wasn't enough power, these transceivers could be used with the Heathkit HA-14 mobile Kompact® Kilowatt 1-KW PEP amplifier (HOM #58).

73, from AF6C



This article originally appeared in the June 2016 issue of RF, the newsletter of the Orange County Amateur Radio Club - W6ZE.

Remember, if you are getting rid of any old Heathkit Manuals or Catalogs, please pass them along to me for my research.

Thanks - AF6C